
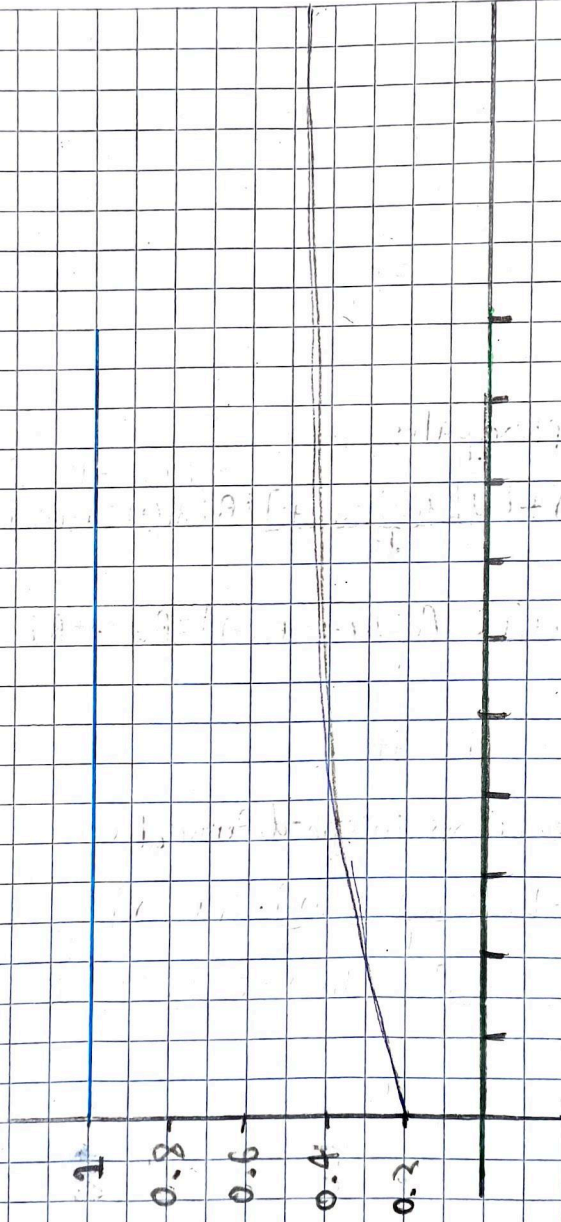


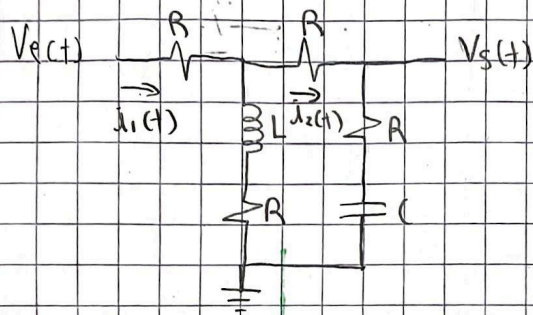$P_{\text{auct}} - P_{\text{AUC}} - \text{Chand 4}$





Ecuaciones principales

$$V_e(t) = R i_1(t) + L \frac{d[i_1(t) - i_2(t)]}{dt} + R [i_1(t) - i_2(t)]$$

$$L \frac{d[i_1(t) - i_2(t)]}{dt} + R [i_1(t) - i_2(t)] = R i_2(t) + R i_2(t) + \frac{1}{C} \int i_2(t) dt$$


$$V_e(t) = R i_2(t) + \frac{1}{C} \int i_2(t) dt$$


Modelo de ecuaciones integro-diferenciales


$$i_1(t) = [V_e(t) - L \frac{d[i_1(t) - i_2(t)]}{dt} + R i_2(t)] \frac{1}{2R}$$

$$i_2(t) = [L \frac{d[i_1(t) - i_2(t)]}{dt} + R i_1(t) - \frac{1}{C} \int i_2(t) dt] \frac{1}{3R}$$
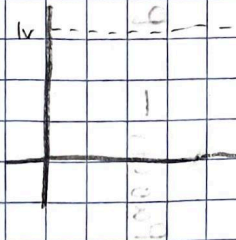
$$V_e(t) = R i_2(t) + \frac{1}{C} \int i_2(t) dt$$



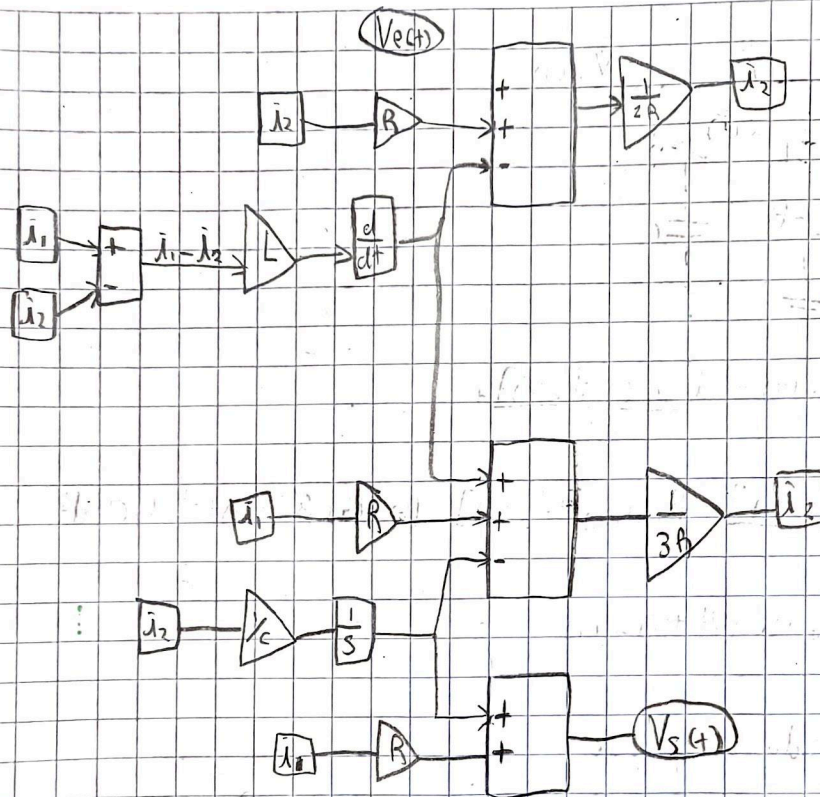

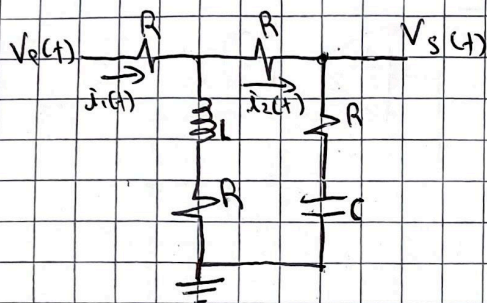

$$V_e(t) = R i_1(t) + L \frac{d[i_1(t) - i_2(t)]}{dt}$$

$$L \frac{d[i_1(t) - i_2(t)]}{dt} + R[i_1(t) - i_2(t)] = R i_2(t) + R \int i_2(t) dt$$

$$V_s(t) = \frac{1}{C} \int i_2(t) dt + R i_2(t)$$

Transformada de Laplace

$$V_e(s) = R I_1(s) + L S[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)]$$

$$L S[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)] = R I_2(s) + R \frac{I_2(s)}{s}$$

$$V_s(s) = R I_2(s) + \frac{I_2(s)}{s}$$

Procedimiento algebraico

$$V_e(s) = (R + LS + R)I_1(s) - (LS + R)I_2(s)$$

$$= (LS + 2R)I_1(s) - (LS + R)I_2(s)$$

$$LSI_1(s) - LS I_2(s) + R I_1(s) - R I_2(s) = 2R I_2(s) + \frac{I_2(s)}{Cs}$$

$$LS I_1(s) + R I_1(s) = 3R I_2(s) + LS I_2(s) + \frac{I_2(s)}{Cs}$$

$$(LS + R)I_1(s) = (3R + LS + \frac{1}{Cs})I_2(s)$$

$$I_1(s) = \frac{3RS + (LS^2 + 1)I_2(s)}{Cs(LS + R)} = \frac{(LS^2 + 3RS + 1)I_2(s)}{Cs(LS + R)}$$

$$V_e(s) = \frac{(LS + 2R)(LS^2 + 3RS + 1)I_2(s)}{Cs(LS + R)} - (LS + R)I_2(s)$$

$$= \left[\frac{(LS + 2R)(LS^2 + 3RS + 1) - Cs(LS + R)(LS + R)}{Cs(LS + R)} \right] I_2(s)$$

$$CL^2S^3 + 3CLRS^2 + LS + 2CLR + 6CR^2S + 2R$$

$$- CL^2S^3 - 2CLRS^2 - CR^2S$$

$$V_e(s) = \frac{3CLR S^2 + (5CR^2 + L)S + 2R}{Cs(LS + R)}$$

$$V_s(s) = \frac{CRS + 1}{Cs} I_2(s)$$

$$\frac{3CLR S^2 + (5CR^2 + L)S + 2R}{Cs(LS + R)}$$

$$\frac{V_s(s)}{V_e(s)} = \frac{CLR S^2 + (CR^2 + L)S + R}{3CLR S^2 + (5CR^2 + L)S + 2R}$$

$$(CRS + 1)(LS + R) = CLR S^2 + CR^2S + LS + R$$

$$num = (C1.7E-6) * (3.3E-3) * (3.3E3) / (4.7E-6) * (3.3E3) * 2 + 3.3E-3, 3.3E3$$

$$R = 3.3E3$$

$$L = 1.5E-3$$

$$C = 4.7E-6$$

Estabilidad en lazo abierto

Calcular los polos de la función de transferencia

$$V_{sc}(s) = \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R}$$

$$\text{den} = [3 * L * R, 5 * C * R^2 + L, 2 * R]$$


$L = \text{hp.roots}(\text{den})$

→ FPrint: Las raíces son $\{L[0]\}$ y $\{L[1]\}$

$$\lambda_1 = -3666,662 \cdot 368$$

$$\lambda_2 = -25.790$$

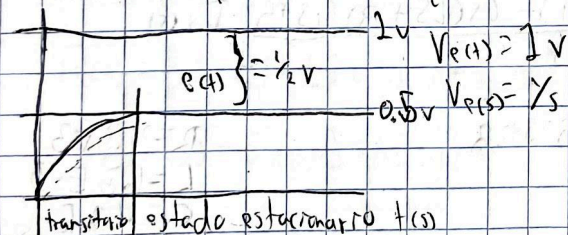El sistema presenta una respuesta estable y sobreamortiguada



Error en estado estacionario

$$e(s) = \lim_{s \rightarrow 0} s \cdot V_{e(s)} \left[1 - \frac{V_{s(s)}}{V_{e(s)}} \right]$$

$$= \lim_{s \rightarrow 0} s \cdot \frac{1}{s} \left[1 - \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R} \right]$$

$$= \frac{R}{2R}$$

$$e(t) = \frac{1}{2} V$$